


Comp3402 The Full Adder

C.B.Price January 2024

Purpose	(i) To learn how to use the Structural Architecture, (ii) To apply this to construct a full adder
Files Required	Vivado software (on machines, free download) and zipped projects
ILO Contribution	LO 5
Send to Me	nix
Homework	Read chapter 13

1. Prep for coding the Adder Bit-Slice

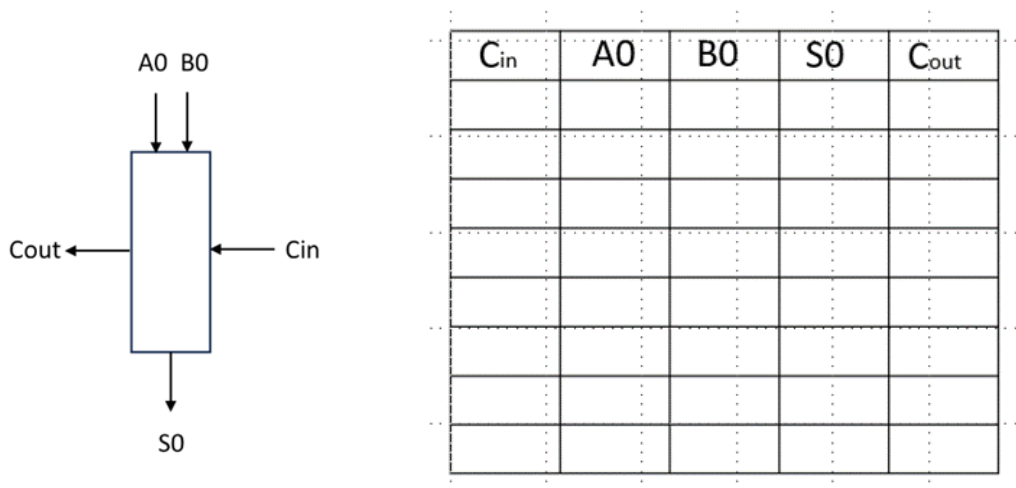(a) Here's a single bit slice which has three inputs, C_{in} , A_0 and B_0 and two outputs, the sum S_0 and carry out C_{out} . Create the truth table for all 8 possible input values.



(b) Look at the rows where $S_0 = 1$. Create a logical mini-term for each row. E.g., if you have a row with $C_{in}=0$, $A_0 = 1$, $B_0 = 0$, then the mini-term will be $A \cdot \sim B \cdot \sim C$.

(c) Combine the 4 mini-terms to create a logical expression for $S_0 =$

(d) Repeat (b) and (c) to get an expression for C_{out} .

2. Coding the Adder Bit-Slice


(a) Fire up Vivado and open the source file **fullAdderSlice.vhd**. You will see that 8 mini-terms have been declared for you, the first 4 are for the sum and terms 5-8 are for the carry.

(b) Code your expressions for the 8 mini-terms you have found above. Here's an example how to code the mini-term $A \cdot \sim B \cdot \sim C$: **A and not(b) and not(C)**.

(c) Now code the expressions for sum **S** and for **Cout**. Do not attempt to synthesise, we must complete the second source file.

 3. Assembling the complete 4-bit Adder.

Here's the *structure* of our 4-bit adder made from 4 of the Adder Bit-Slices you have just coded.



(a) Open up the source file **FourBit_Full_Adder.vhd** where the Structural Architecture is used. You will see the following code which defines the **Component fullAdderSlice**.

```
COMPONENT fullAdderSlice
] Port (A : in std_logic;
      B : in std_logic;
      Cin : in std_logic;
      S : out std_logic;
      Cout : out std_logic);
- END COMPONENT;
```

The code which defines how the bit-slice components are connected is shown in the following begin-end block, though this is incomplete

```
BEGIN
stage0: fullAdderSlice PORT MAP ( X(0), Y(0), Cin, S(0), C(1) );
stage1: fullAdderSlice PORT MAP ( , , , , );
stage2: fullAdderSlice PORT MAP ( , , , , );
stage3: fullAdderSlice PORT MAP ( , , , , Cout );
END Structural ;
```

Fill in the missing signals. You need to use signals from the **Entity FourBit_Full_Adder** declared up top, specifically in the **Port**.

(b) Now it's time to synthesise the whole circuit.

4. Running the TestBench

Run the associated test-bench to check the synthesis. You might like to change the radix of the display so it shows unsigned decimals. You can do this by right-clicking on the value fields:

